

4. a) $P_{elec}(s) = \frac{V_s(s)}{V_c(s)} = \frac{V_a}{V_c} \cdot \frac{I_c}{V_a} \cdot \frac{V_s}{I_c}$

$$\frac{V_a}{V_c} = s \quad \frac{V_s}{I_c} = s \cdot R_s = 1$$

$$I_c = \frac{V_a - V_{emf}}{L_c s + R_c}$$

$$V_{emf} = K_f x s$$

$$F = K_f I_c = b x s + k_i x + m x s^2$$

$$x = \frac{K_f I_c}{m s^2 + b s + k_i} \quad \text{so, } V_{emf} = \frac{K_f^2 I_c s}{m s^2 + b s + k_i}$$

$$\text{Thus, } \frac{I_c}{V_a} = \frac{1}{(L_c s + R_c) \left(1 + \frac{K_f^2 s}{(m s^2 + b s + k_i)(L_c s + R_c)} \right)}$$

$$\boxed{\frac{V_s}{V_c} = \frac{s}{(L_c s + R_c) \left(1 + \frac{K_f^2 s}{(m s^2 + b s + k_i)(L_c s + R_c)} \right)}}$$

$$\begin{aligned} \text{b) } P_{elec} &= \frac{V_s}{V_c} = \frac{V_a}{V_c} \cdot \frac{I_c}{V_a} \cdot \frac{V_s}{I_c} \\ &= s \cdot \frac{1}{L_c s + R_c} \cdot 1 \\ &= \boxed{\frac{s}{L_c s + R_c}} \end{aligned}$$

c) At high frequencies, both transfer functions will be the same because $\lim_{s \rightarrow \infty} \frac{K_f^2 s}{(m s^2 + b s + k_i)(L_c s + R_c)} = 0$

Thus, any affect $V_{backemf}$ has disappears

d) To obtain DC gain of $G_u = -0.5 \text{ A/V}$, set $s=0$ for C.L. TF

$$\text{so, } \frac{-R_2}{R_1} \cdot \frac{1}{1+L} \cdot -SR_s \Rightarrow \frac{R_2}{10,000} \cdot 0.2 = \frac{1}{10}$$

$$R_2 = 5,000 \Omega$$

To obtain a gain cross over frequency of $\omega_c = 6 \times 10^5$ rad/sec, we set the zero of C_{eqc} a decade before desired ω_c and the pole of C_{eqc} a decade after desired ω_c .

Therefore,

$$\begin{aligned} R_3 &= 121,000 \Omega \\ C_1 &= 1.3 \times 10^{-9} \text{ F} \\ C_2 &= 1.3 \times 10^{-12} \text{ F} \end{aligned}$$